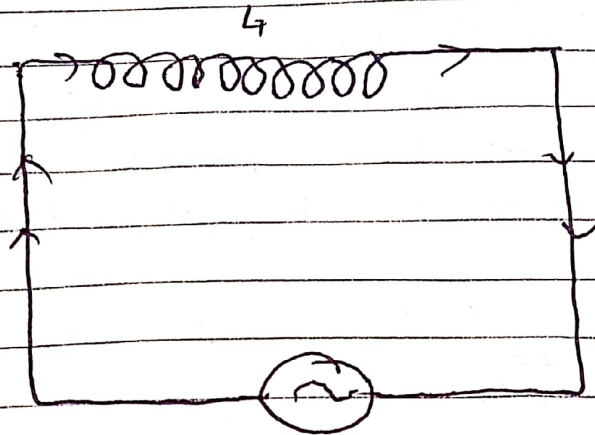


A.c. Containing Inductor only:-



Let the instantaneous voltage be

$$V = V_0 \sin \omega t$$

Let if I be the linked current to coil at any instant

$$E = -L \frac{dI}{dt}$$

$$E = -V$$

$$V = -E$$

$$V = +L \frac{dI}{dt}$$

$$\frac{V}{L} dt = dI$$

$$dI = \frac{V_0}{L} \sin \omega t dt$$

$$\int dI = \frac{V_0}{L} \int \sin \omega t dt$$

$$I = \frac{V_0}{L} \left[-\frac{\cos \omega t}{\omega} \right]$$

$$\sin(90 - \theta) = \cos \theta$$

$$\sin(\theta - 90) = -\cos \theta$$

PAGE NO.:

DATE:

$$I = \frac{V_0}{\omega L} [-\cos \omega t]$$


$$I = \frac{V_0}{\omega L} \sin(\omega t - \frac{\pi}{2})$$

The maximum or peak value of the current is I_0 , $\sin(\omega t - \frac{\pi}{2})$


$$I_0 = \frac{V_0}{\omega L}$$

$$I = I_0 \sin(\omega t - \frac{\pi}{2})$$

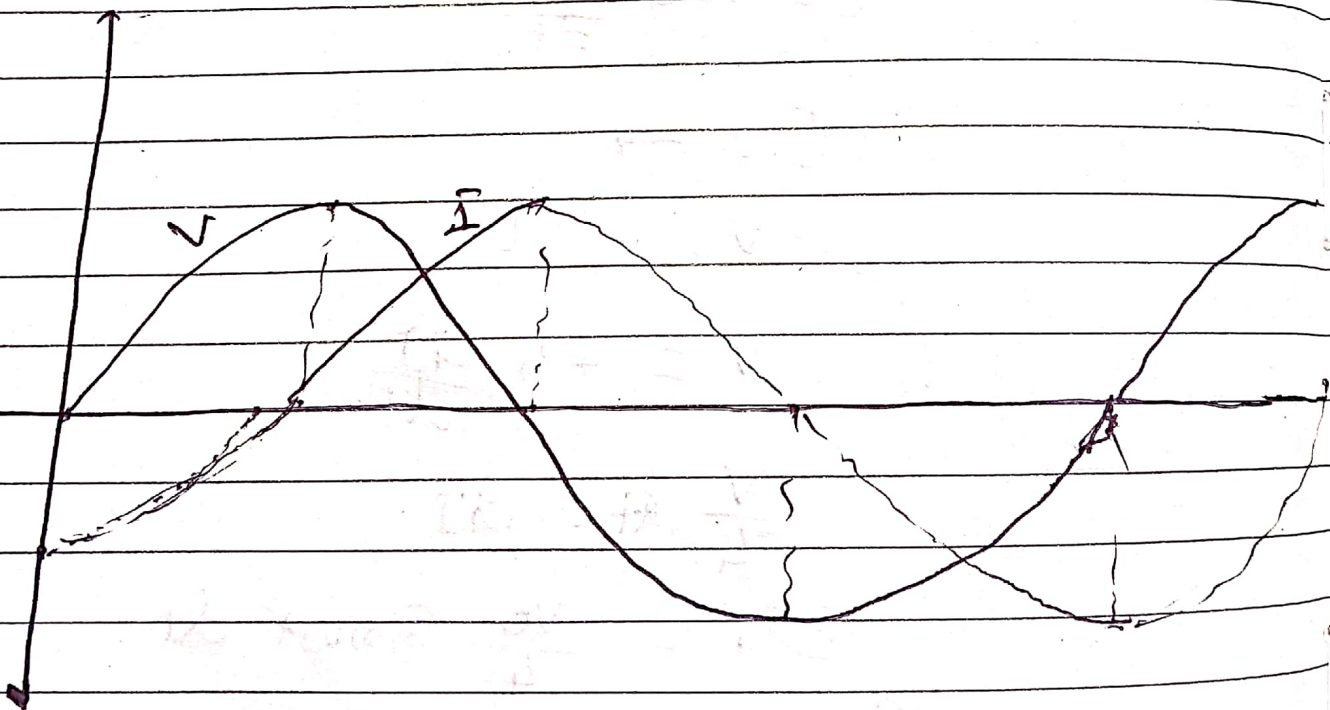The current is lagging by a phase of $\frac{\pi}{2}$ to voltage



Phasor diagram:-

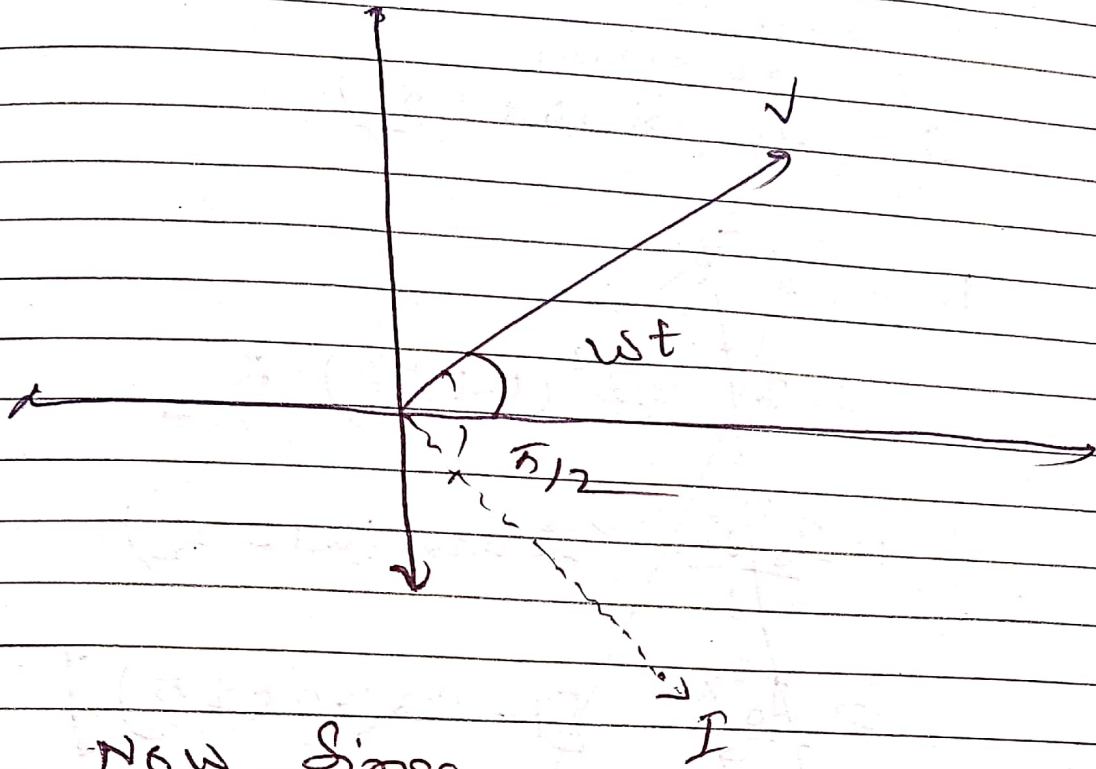

NOW Since

$$I_0 = \frac{V_0}{\omega L}$$

$$\textcircled{a} \frac{V_0}{I_0} = \omega L$$

$\frac{V_0}{I_0}$ it appears as resistance to the circuit and it is called Inductive reactance

$$X_L = \omega L$$

Avg power in inductor or capacitor is zero

$$V = V_0 \sin \omega t$$

$$I = I_0 \sin(\omega t \pm \frac{\pi}{2})$$

~~$$P = I^2 R$$~~

~~$$= I_0^2 \sin^2(\omega t \pm \frac{\pi}{2}) R$$~~

~~$$= \frac{I_0^2 R}{2} [1 - \cos(2\omega t \pm \pi)]$$~~

~~$$= \frac{I_0^2 R}{2} [1 - \cos(2\omega t \pm \pi)]$$~~

$$P_{av} = \langle P \rangle$$

$$= \frac{I_0^2 R}{2} [1 - \langle \cos(2\omega t \pm \pi) \rangle]$$

$$\langle \cos(2\omega t \pm \pi) \rangle = 0$$

$$P = VI$$

$$P = I_0 V_0 \sin \omega t \sin (\omega t \pm \frac{\pi}{2})$$

$$= \frac{V_0 I_0}{2} [2 \sin \omega t \sin (\omega t \pm \frac{\pi}{2})]$$

$$[2 \sin A \sin B = \cos (A-B) - \cos (A+B)]$$

$$P = \frac{V_0 I_0}{2} [\cos (\frac{\pi}{2}) - \cos (2\omega t \pm \pi)]$$

$$= \frac{V_0 I_0}{2} \cos (2\omega t \pm \pi)$$


$$P_{av} = - \frac{V_0 I_0}{2} \langle \cos (2\omega t \pm \pi) \rangle$$

$$\langle \cos (2\omega t \pm \pi) \rangle = 0$$

$$P_{av} = - \frac{V_0 I_0}{2} \times 0$$

$$P_{av} = 0$$

A.c Containing L-e-R

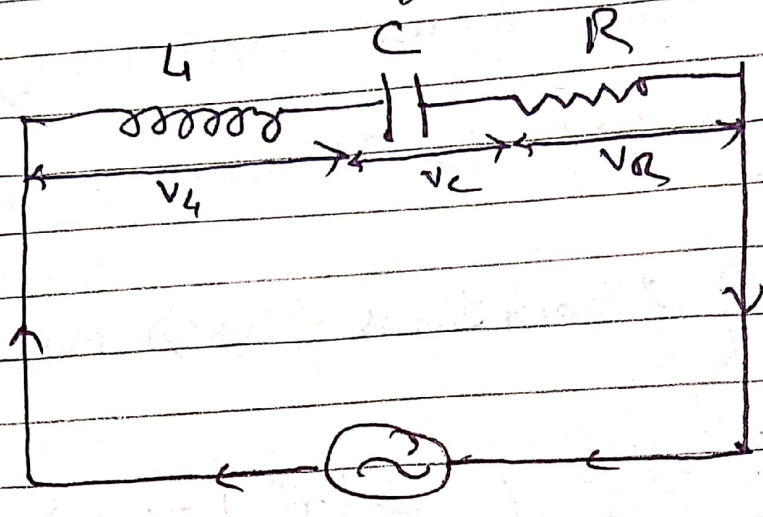


Let the instantaneous voltage be

$$V = V_0 \sin \omega t$$

then voltage will be distributed in series

$$\vec{V} = \vec{V}_L + \vec{V}_C + \vec{V}_R$$

($V_L > V_C$)

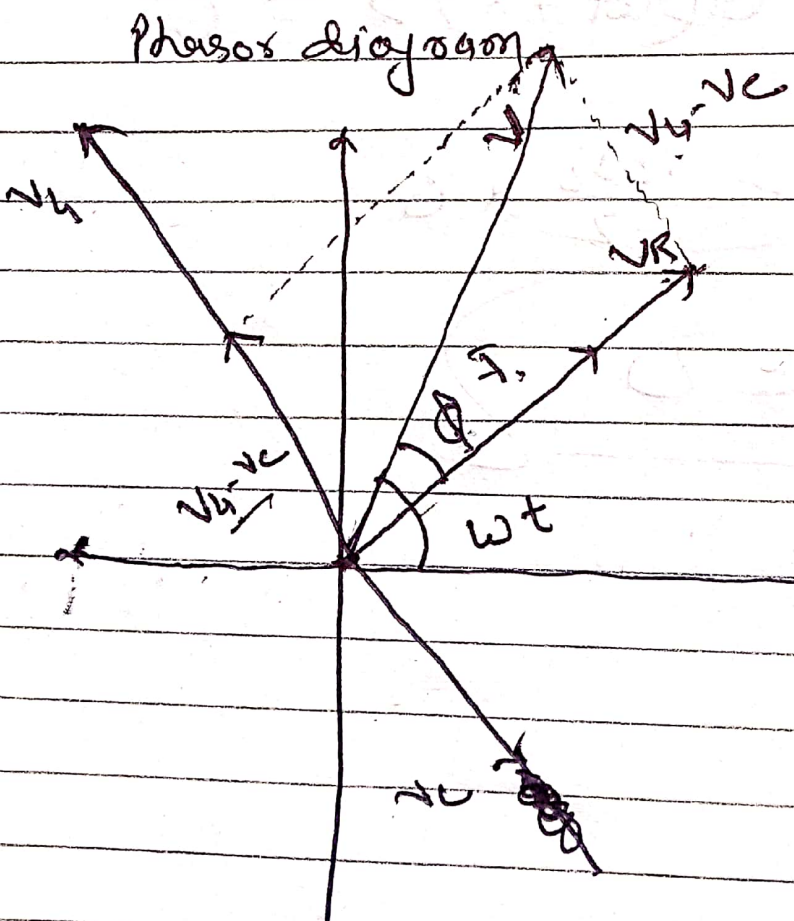

Let I be the instantaneous value of current

$$V_L = I X_L \quad V_C = I X_C \quad V_R = IR$$

$$V = \sqrt{(V_L - V_C)^2 + V_R^2}$$

$$V = \sqrt{(IX_L - IX_C)^2 + I^2 R^2}$$

$$V = I \sqrt{(X_L - X_C)^2 + R^2}$$

$$\frac{V}{I} = \sqrt{(X_L - X_C)^2 + R^2}$$

$\frac{V}{I}$ is like Resistance of the combination. It is called Impedance represented by Z

$$\frac{V}{I} = Z$$

$$Z = \sqrt{(X_L - X_C)^2 + R^2}$$

Now

$$I = I_0 \sin(\omega t - \phi)$$

$$\tan \phi = \frac{V_L - V_C}{V_R} = \frac{IX_L - IX_C}{IR}$$

$$\tan \phi = \frac{X_L - X_C}{R}$$