

Resonance in Series L-C-R:-

If in any ~~R~~ L-C-R Circuit

$$\underline{V_L = V_C}$$

$$\underline{I X_L = I X_C}$$

$$\underline{X_L = X_C}$$

$$\underline{X_L - X_C = 0}$$

Reactance of circuit ≈ 0

$$Z = \sqrt{(X_L - X_C)^2 + R^2}$$

$$\boxed{Z = R}$$

\therefore impedance of the circuit will become ~~zero~~ minimum

$$I = \frac{V}{Z} = \frac{V}{R} \text{ (Maximum)}$$

\therefore it is the state of Resonance.

Resonant frequency:-

$$X_L = X_C$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$2\pi f = \frac{1}{\sqrt{LC}}$$

$$\boxed{f = \frac{1}{2\pi\sqrt{LC}}}$$

Sharpness of Resonance:-

We know

$$I_0 = \frac{V_0}{\sqrt{(X_L - X_C)^2 + R^2}}$$

In state of resonance 2-2

$$I_0^{\max} = \frac{V_0}{R}$$

$\omega = \omega_0$ (Resonant frequency)

Now, we are choosing two side frequencies $\omega_1 = \omega_0 + \Delta\omega$ and $\omega_2 = \omega_0 - \Delta\omega$ such that the

$$I_0 = \frac{1}{\sqrt{2}} I_0^{\max}$$

$$I_0 = \frac{V_0}{\sqrt{(X_L - X_C)^2 + R^2}}$$

$$= \frac{1}{\sqrt{2}} I_0^{\max} = \frac{V_0}{\sqrt{2}R}$$

$$\Rightarrow \sqrt{(X_L - X_C)^2 + R^2} = \sqrt{2}R$$

$$(X_L - X_C)^2 + R^2 = 2R^2$$

$$(x_4 - x_c)^2 = R^2$$

$$x_4 - x_c = R$$

$$w_4 - \frac{1}{w_c} = R$$

$$(w_0 + \Delta w)_4 - \frac{1}{(w_0 + \Delta w)_c} = R$$

$$w_0 4 \left(1 + \frac{\Delta w}{w_0}\right) - \frac{1}{w_0 c \left(1 + \frac{\Delta w}{w_0}\right)} = R$$

$$w_0 4 \left(1 + \frac{\Delta w}{w_0}\right) - \frac{w_0 4}{\left(1 + \frac{\Delta w}{w_0}\right)} = R$$

$$w_0 4 \left[\left(1 + \frac{\Delta w}{w_0}\right) - \left(1 + \frac{\Delta w}{w_0}\right)^{-1} \right] = R$$

$$\frac{\Delta w}{w_0} \ll 1$$

$$(1+x)^n \approx 1+nx$$

$$w_0 4 \left[\left(1 + \frac{\Delta w}{w_0}\right) - \left(1 - \frac{\Delta w}{w_0}\right) \right] = R$$

$$w_0 4 \frac{2 \Delta w}{w_0} = R$$

$$4 \Delta w = R$$

$$\Delta w = \frac{R}{4}$$

Sharpness of Resonance


$$Q = \frac{\omega_0}{\Delta\omega}$$

$$Q = \frac{\omega_0 L}{R} = \frac{X_L}{R}$$

or

$$Q = \frac{1}{\omega_0 C R} = \frac{X_C}{R}$$

L-C Oscillation

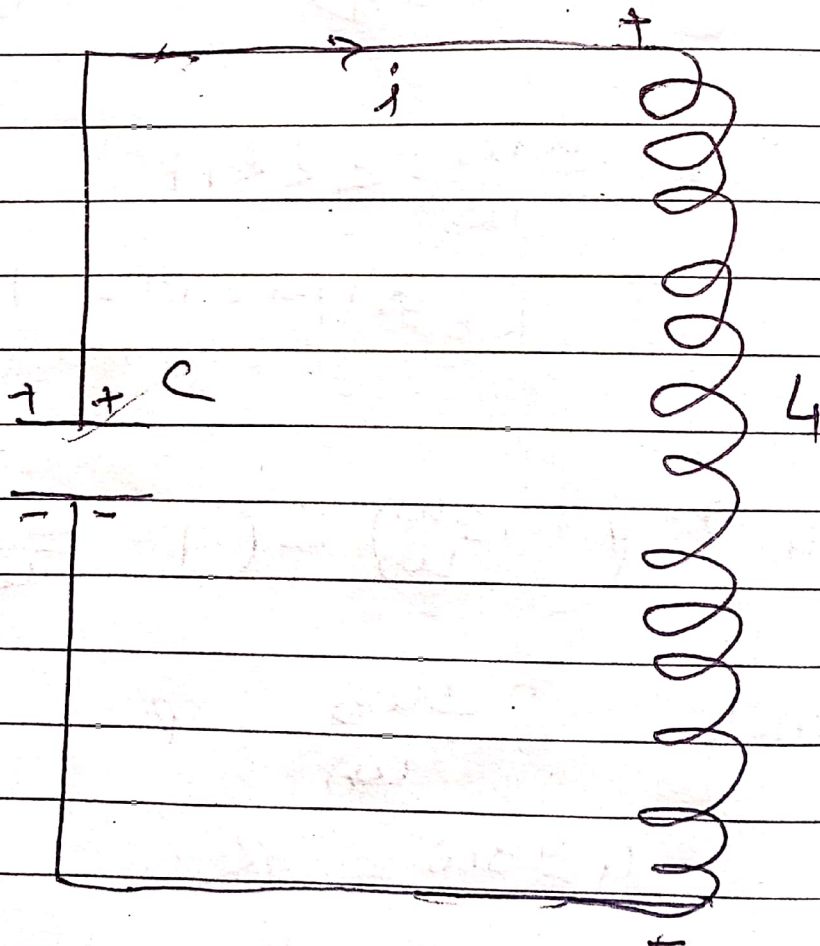

A Capacitor of capacitance 'C' when fully charged is connected to Inductor 'L' when charge discharges then back e.m.f is developed

$$V_C + V_L = 0$$

~~$$\frac{Q}{C} - L \frac{dI}{dt} = 0$$~~

$$\frac{Q}{C} - \frac{dI}{dt} = 0$$

~~$$\frac{dI}{dt}$$~~

$$I = -\frac{dQ}{dt} \quad \frac{dI}{dt} = -\frac{d^2Q}{dt^2}$$

$$\frac{Q}{C} + \frac{d^2Q}{dt^2} = 0$$

$$\frac{d^2Q}{dt^2} + \frac{1}{LC} Q = 0$$

$$\frac{d^2Q}{dt^2} + \omega^2 Q = 0$$

$$\frac{d^2Q}{dt^2} = -\omega^2 Q$$

③ in comparison to

$$\frac{d^2x}{dt^2} = -\omega^2 x$$

for S.H.M.

Flow of charge will execute
S. H. M.

$$Q = Q_0 \cos \omega t$$

$$I = - \frac{dQ}{dt}$$

$$= - Q_0 \frac{d \cos \omega t}{dt}$$

$$I = + Q_0 \omega \sin \omega t$$

$$\sin \omega t = 1$$

$$I_0 = Q_0 \omega$$

$$I = I_0 \sin \omega t$$

Stored electric energy at any instant

$$U_E = \frac{Q^2}{2C} \quad (U_{E(\max)} = \frac{Q_0^2}{2C})$$

Stored magnetic energy at any instant

$$U_m = \frac{1}{2} L I^2$$

$$U_m(\max) = \frac{1}{2} L I_0^2$$